
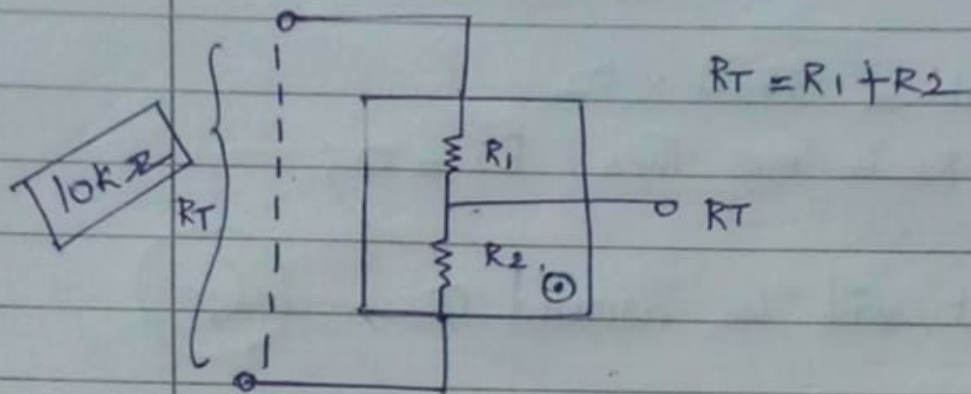


Module - 12 POTENTIOMETER

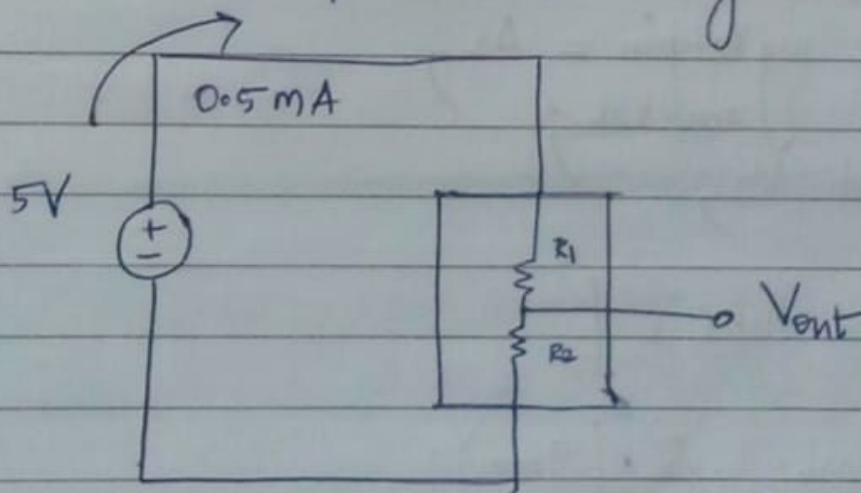

- ① When $R_2 = 0$ • $R_1 = R_T = 10k\Omega$
- ② When $R_2 = 5k\Omega$; $R_1 = 5k\Omega$
- ③ $R_1 = 0$; $R_2 = R_T = 10k\Omega$

Let's make simple circuit Analysis :



$$I = \frac{V}{R} = \frac{5V}{10k} = 0.5 \text{ mAmps}$$


$$0.5 \times 10^{-3} A$$

$$V_{out} = I \times (R_{Total})_2$$

$$V_{out} = 5mA \times R_2$$


if R_2 is low then $R_2 = 0$;

- V_{out} will be around 0.

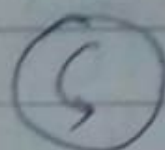

if R_2 is Rised and turned to Max

- V_{out} will be around 5V.

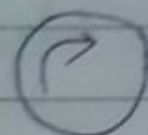

Therefore the V_{out} will be around 0-5V

```
int myVoltPin = A2;
int readVal;
float V2;
```


```
void setup() {
```

```
  Serial.begin(9600);
}
```

```
void loop() {
```

```
  readVal = analogRead(myVoltPin);
  V2 = (5.0 / 1023.0) * readVal;
}
```

Voltage divider circuit

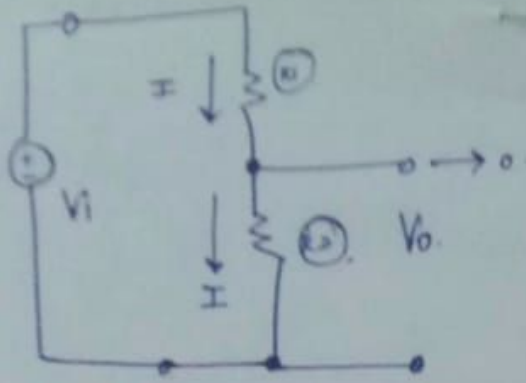

Equating ① & ②

$$\frac{V_{in}}{R_1 + R_2} = \frac{V_o}{R_2}$$

$$V_o = \frac{V_{in} \cdot R_2}{R_1 + R_2}$$

Ohms Law


$$V = IR$$

$$V_i = I(R_1 + R_2)$$

$$I = \left(\frac{V_{in}}{R_1 + R_2} \right) \quad \text{--- ①}$$

$$V_o = I R_2$$
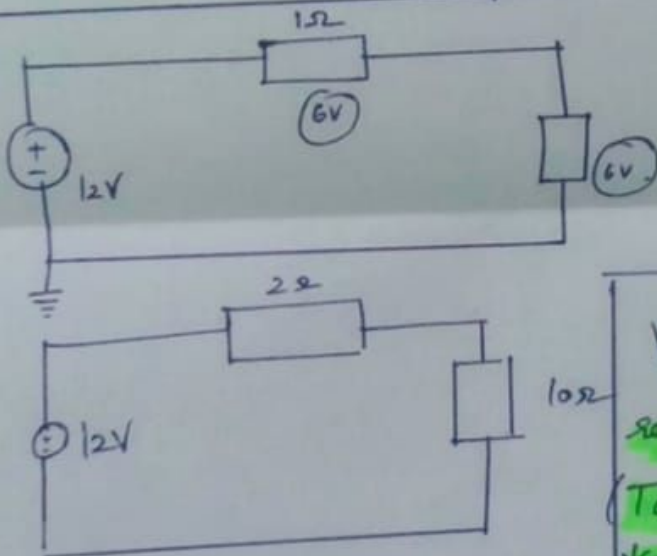
$$I = \left(\frac{V_o}{R_2} \right) \quad \text{--- ②}$$



Voltage across 2Ω

$$= \frac{12}{12} \times 2\Omega = 2 \text{ Volts}$$

Voltage across 10Ω

$$= \frac{12}{12} \times 10 \text{ V} = 10 \text{ Volts}$$

Voltage across any resistor =
 $\left(\frac{\text{Total Voltage}}{\text{Total Resis}} \right) \times \text{Resistor of concern}$

$$R_2 = R_1 \times \frac{\text{Desired } V_{out}}{(V_{in} - V_{out})}$$